

Assignment 3

Due October 22, 17:00


NOTE: Late submissions will **NOT** be accepted. Please submit a single PDF file with your answers via the **ECE 355 Brightspace** webpage.

1. [10 points] Solve Problem **7.11** from the textbook.

2. [5 points] Suppose some FSM has 3 inputs, internal **Ready**, external bus-grant **Grant**, and external bus-free **Free** signals, as well as 2 outputs, bus-request **Req** and bus-lock **Lock** signals. Show its Moore-type state diagram, assuming that the FSM implements the following bus protocol: (1) initially, the FSM outputs **Req** = **0** and **Lock** = **0** and waits for both **Ready** and **Free** to be asserted; (2) After receiving **Ready** = **1** and **Free** = **1**, the FSM outputs **Req** = **1** and **Lock** = **0** and waits for **Grant** to be asserted; (3) After receiving **Grant** = **1**, provided that both **Ready** and **Free** still equal **1**, the FSM outputs **Req** = **0** and **Lock** = **1** and waits for **Ready** to become **0**; once **Ready** = **0**, the FSM returns to step (1).

NOTE: Should **Ready** and/or **Free** become **0** while waiting for **Grant** = **1**, the FSM returns to step (1). The FSM ignores the **Grant** input in steps (1) and (3), and it ignores the **Free** input in step (3).

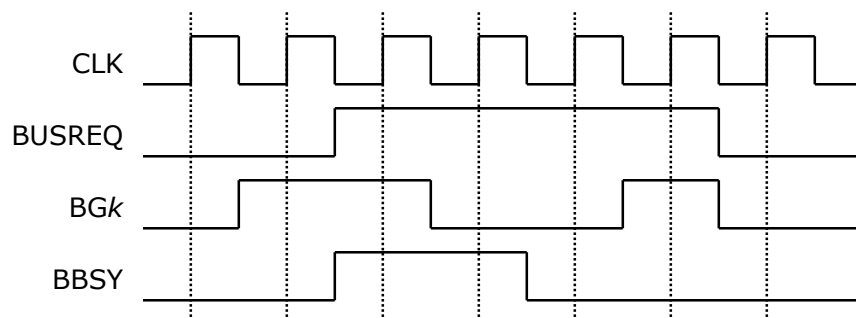3. [5 points] Recall the Mealy FSM state diagram on **Slide 32** of the “**Interfacing**” lecture notes, where the circuit is initially in state **Idle**. Given the input waveform shown below, draw the corresponding output waveforms.



4. [5 points] Consider the daisy-chain arbitration scheme shown below. Assume that the input-to-output signal propagation delays are the same and equal to **d** for all three devices, the inverter, and the **AND** gate. Also, assume that device **x** is able to start using the bus (making **/BRx** = **1** and **/BBSY** = **0**) only when it receives a 0-1 transition on its bus-grant input **BGx** and detects that the bus is not currently busy (i.e., **/BBSY** = **1**). Also, assume that device **x** lets the bus-grant propagate through only when it is neither requesting nor using the bus. Finally, assume that any of the three devices will need to use the granted bus for only **3d** time units. Complete the timing diagram shown on the next page.

